

VERILOG CODE FOR FULL ADDER

```
//Full adder using structural modeling

module full_adder_s (
    input a,b,cin,
    output sum,carry
);

wire w1,w2,w3,w4;      //Internal connections

xor(w1,a,b);

xor(sum,w1,cin);        //Sum output

and(w2,a,b);


and(w3,b,cin);

and(w4,cin,a);



or(carry,w2,w3,w4);     //carry output

endmodule
```


OUTPUT WAVEFORM:

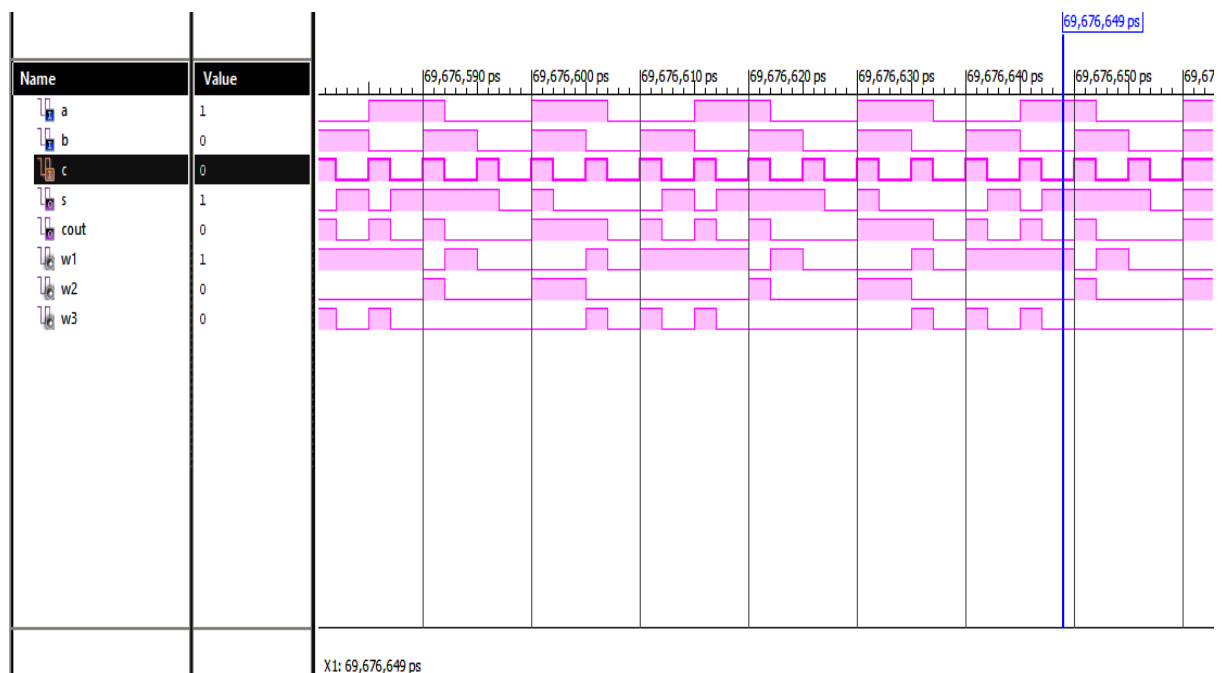

Rtl schematic view:

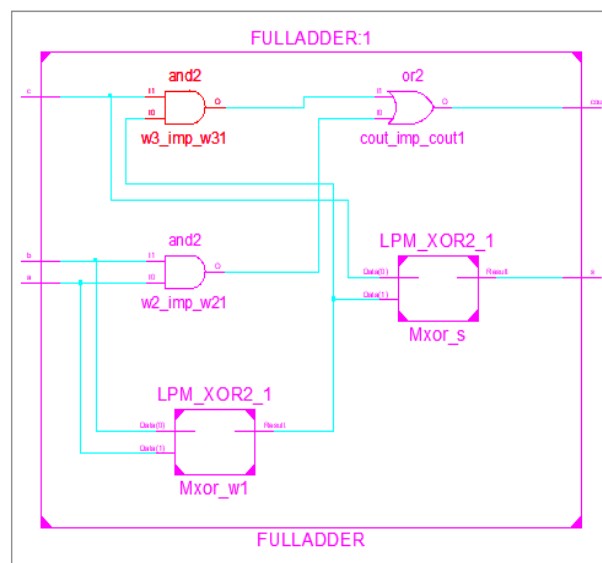 

Technology schematic view:

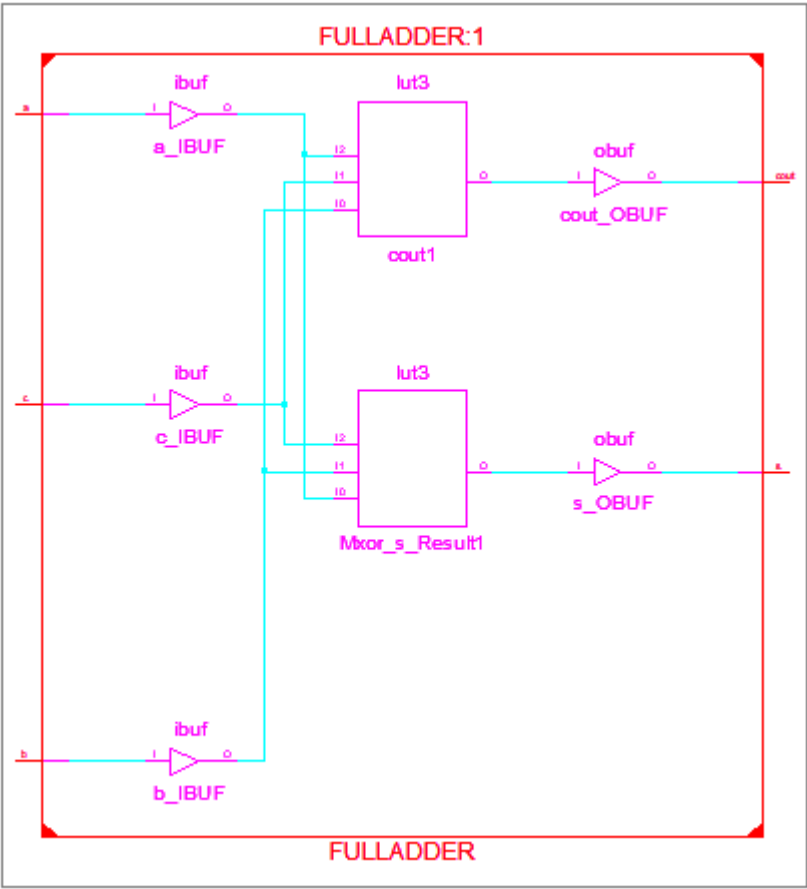

Device Utilization Summary (estimated values)				[+]
Logic Utilization	Used	Available	Utilization	
Number of Slices	1	2448	0%	
Number of 4 input LUTs	2	4896	0%	
Number of bonded IOBs	5	172	2%	

Timing Summary:

Speed Grade: -4

Minimum period: No path found

Minimum input arrival time before clock: No path found


Maximum output required time after clock: No path found

Maximum combinational path delay: 6.236ns


VERILOG CODE FOR D-FLIP FLOP


```
module flipflop(d,clk,clr,q,qb);  
  
input d,clk,clr;  
  
output reg q;  
  
output qb;  
  
assign qb=~q;  
  
always@(posedge clk)  
  
begin  
  
if(clr==1)  
  
q=0;  
  
else  
  
q=d;  
  
end  
  
endmodule
```

OUTPUT WAVEFORM:

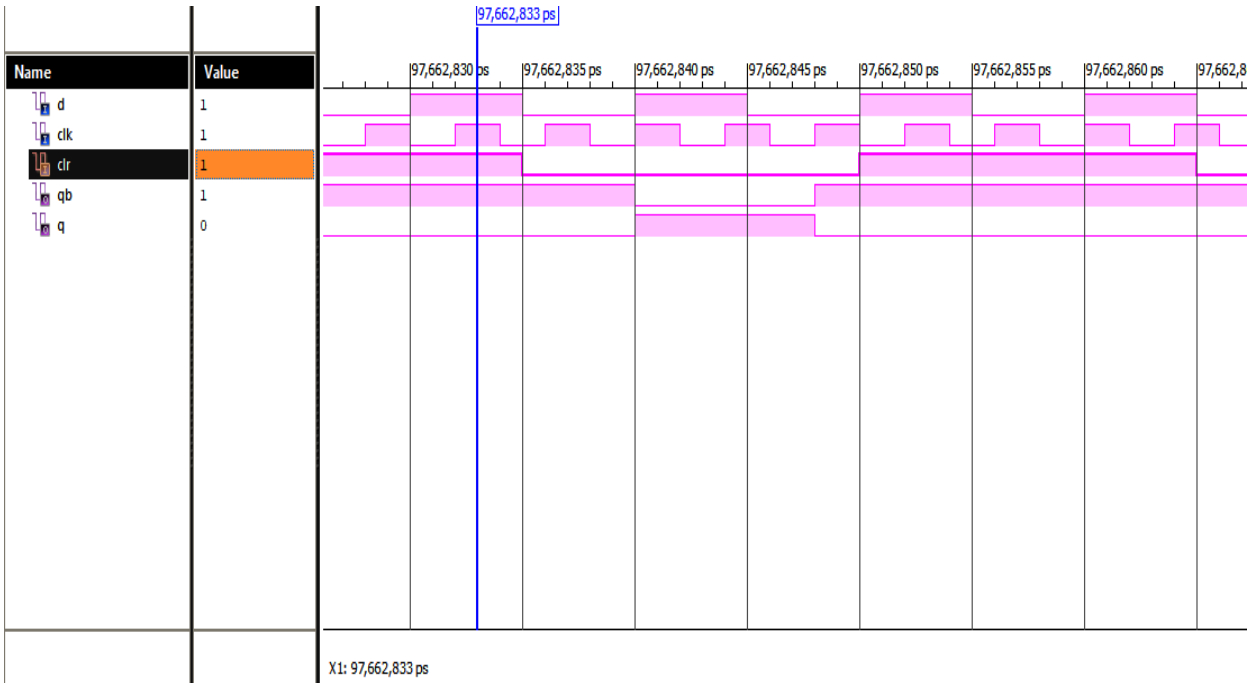


Rtl schematic view:

 

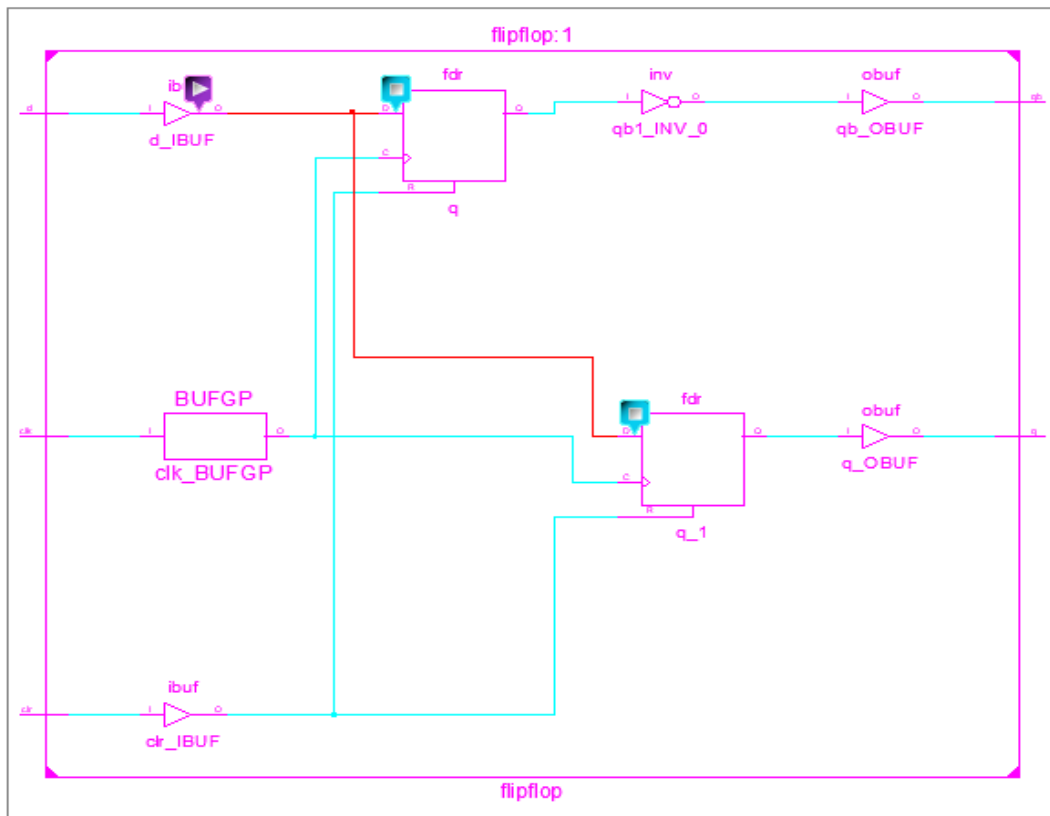

Technology schematic view:

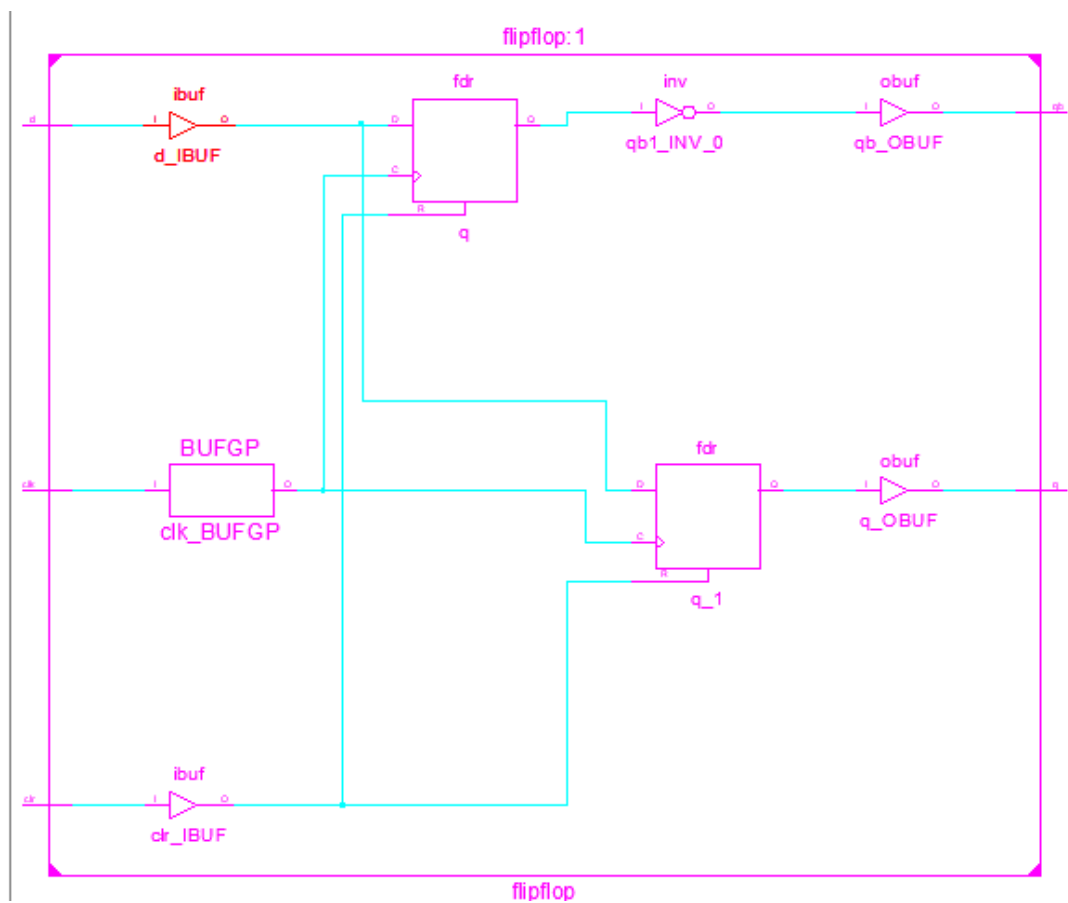

Device Utilization Summary (estimated values)				[-]
Logic Utilization	Used	Available	Utilization	
Number of Slices	1	2448	0%	
Number of 4 input LUTs	1	4896	0%	
Number of bonded IOBs	5	172	2%	
Number of GCLKs	1	24	4%	

Timing Summary:

Speed Grade: -4

Minimum period: No path found

Minimum input arrival time before clock: 2.576ns

Maximum output required time after clock: 5.407ns

Maximum combinational path delay: No path found